

Chapter 13

Alternating Current Circuits

**Chapter 13 is mostly finished, but is not in camera-ready format.
This file doesn't have any of the diagrams, but it does have
some text-excerpts, with omissions indicated by**

background: This chapter assumes you have studied Sections 11.10 (RC circuits) & 12.5 (LR circuits).

strategy: Read Sections 13-1 & 13-2 first. Then, if your class studies the time-dependency of voltage and phasor diagrams (or if you're curious and want to learn), read Sections 13.3 and 13.4.

13.1 Alternating Current

Chapter 11 described the behavior of capacitors & resistors in *direct current* (dc) circuits, where negatively-charged electrons always move in one direction, away from the battery's negative terminal toward its positive terminal.

As described in Section 12.4, electric generators at a power plant produce voltage whose magnitude and direction varies as shown by the *sine curve* on the first graph below. This alternating voltage causes *alternating current* (ac). In an *ac circuit*, electrons move one direction and then the opposite direction, as shown in the second graph, oscillating back and forth about relatively fixed positions.

[two graphs will be shown here]

Over one full cycle, ac voltage is positive for $\frac{1}{2}$ cycle and negative for $\frac{1}{2}$ cycle. A sine curve is symmetric, so the + and - voltages cancel each other and V_{average} is zero. But taking the *root mean square average* (a technique shown in Problem 13-#) gives $V_{\text{rms}} = V_{\text{max}} / \sqrt{2} = .7071 V_{\text{max}}$. Similarly, $I_{\text{rms}} = .7071 I_{\text{max}}$.

In the United States, most ac current that is delivered to houses and businesses alternates at a rate of 60 cycles per second, with V_{rms} approximately 120 Volts, so $V_{\text{peak}} = V_{\text{rms}} / .707 = 120 / .707 = 170$ Volts.

13.2 Equations for Alternating Current Circuits

The circuit below contains an *ac voltage source* (like an ac generator, or just plugging the circuit into an electrical wall-outlet) with a potential difference of ΔV_S , an *inductor* " " (I don't have the graphic in this file, so I'll just fill the spaces with INDUCTOR" temporarily) with ΔV_L and *inductance L* , and a *resistor* " " with ΔV_R and *resistance R*, and a *capacitor* " " with ΔV_C and *capacitance C*.

[picture of LRC circuit will be here]

The rest of Chapter 13 describes the behavior of this type of *LRC series circuit*.

The current and all four potential differences change throughout the cycle. Graphs of I and ΔV have the "continuous sine wave" shape shown in Section 13.1, with *frequency f* and *angular frequency ω* . As explained in Section 5.4c, $\omega = 2\pi f$.

At some point during each ac cycle, the current reaches a maximum I_{max} . And at some point in the cycle, the voltage across the INDUCTOR, --V-- and +H+ reach a maximum; these maximum voltages are ΔV_{Lmax} , ΔV_{Rmax} and ΔV_{Cmax} .

At any instant of time, current is the same in every part of a simple series circuit. If charge is moving \emptyset at the rate of 2 Coulombs/second through the INDUCTOR, at this instant there is 2 Amps \emptyset through the --V-- , and also 2 Amps \emptyset to and from the +H+ .

But ΔV_{Lmax} , ΔV_{Rmax} and ΔV_{Cmax} always occur at different times, and usually have different magnitudes. The timing of these ΔV -maximums is discussed in Sections 13.3 & 13.4, along with their relationship to ΔV_{Smax} . The magnitudes of the ΔV -maximums are given by the equations below, which each has a format of " $\Delta V = I()$ ".

$$\Delta V_{Lmax} = I_{max} X_L, \quad \text{where } X_L + \omega L \text{ is the } \textit{inductive reactance} \text{ of the INDUCTOR.}$$

$$\Delta V_{Rmax} = I_{max} R, \quad \text{where } R \text{ is the } \textit{resistance} \text{ of the } \text{--V--}.$$

$$\Delta V_{Cmax} = I_{max} X_C, \quad \text{where } X_C + 1/\omega C \text{ is the } \textit{capacitive reactance} \text{ of the } \text{+H+}.$$

$$\Delta V_{Smax} = I_{max} Z, \quad \text{where } Z + \sqrt{R^2 + (X_L - X_C)^2} \text{ is the } \textit{impedance} \text{ of the circuit.}$$

In a dc circuit, R is the "resistance" to current flow. Similarly, in an ac circuit Z shows how much the circuit "impedes" the flow of current.

Each element in a circuit contributes to Z , the total impedance of the circuit. The --V-- contributes resistance R , while INDUCTOR and +H+ contribute "reactances" of X_L and X_C . If you study Sections 13.3 and 13.4, you'll discover why Z is not a simple addition of " $R + X_L + X_C$ ".

R , X_L , X_C and Z have the same units: ohms, Ω .

$\Delta V_L = I_{max} \underline{\omega L}$: This equation shows that an INDUCTOR impedes current most when it has a large inductance L (when it is effective at "fighting") and when the frequency ω is large (when current is changing rapidly, thus producing a large $\Delta I/\Delta t$ to "fight against").

The closer a +H+ comes to holding its full charge, the more it impedes the flow of current. Two factors that help a +H+ reach full charge, and thus impede current, are small C (capacity to hold charge) and small ω (a long time-per-cycle allows charge to flow in one direction for a long time, thus causing a buildup). This is why ω and C are "on the bottom" in the V-formula: $\Delta V_C = I_{max} / \underline{\omega C}$.

For a dc series circuit with $\omega=0$, after a long time INDUCTOR doesn't impede current at all because there are no changes to fight against, but a +H+ stops it completely. The X-equations correctly predict these results: substitution of " $\omega = 0$ " gives $X_L = \omega L = (0)L = 0$ [showing that INDUCTOR doesn't impede current] and $X_C = 1/\omega C = 1/(0)C = \infty$ [showing that +H+ impedes the current infinitely].

If an ac circuit is missing any standard elements (L , R or C) the above equations can still be used; just substitute $L = 0$, $R = 0$, or $C = \infty$.

Resonance

$I_{\max} = \Delta V_{L\max} / Z$, so current in an ac circuit is maximum when Z is minimum. The minimum Z (which is equal to $\sqrt{R^2 + (X_L - X_C)^2}$) occurs at *resonance*, when $X_L - X_C = 0$, when $(\omega L) - (1/\omega C) = 0$, $\omega^2 LC = 1$, and $\omega = \sqrt{1/LC}$:

ac-circuit resonance, with minimum Z and maximum I_{\max} , occurs when

$$\omega_{\text{resonance}} = \sqrt{\frac{1}{LC}} \quad \text{and} \quad f_{\text{resonance}} = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

Units: ω is in radians/s, f is in cycles/second (also called Hertz, abbreviated Hz).

If a circuit is not resonant, resonance can be achieved by varying ω , L or C .

Problem 13-# shows how resonance is used to "tune" a radio or television.

Power

In an LRC circuit, power is dissipated (turned into thermal energy) only in . The **INDUCTOR** and  store and release energy, but don't dissipate it. Because only R (not the entire Z) causes power dissipation, there is a *power factor* of R/Z in ac power formulas. If a circuit could have $R = 0$, $R/Z = 0$, and no energy would be dissipated. For a resonant circuit, $Z = \sqrt{R^2 + 0^2} = R$, and $R/Z = 1$. {Optional: some textbooks describe the power factor as $\cos \phi$, where $\cos \phi = (Z/R)$. The meaning of ϕ is discussed in Section 13.4.}

In a dc circuit, P can be calculated in 3 ways: as IV , I^2R , or V^2/R . To calculate the *rms average power* for a full ac cycle, use any dc power formula, replace I & V with I_{rms} & V_{rms} , replace R with Z , and multiply by the power factor of Z/R :

$$P_{\text{rms}} = I_{\text{rms}} V_{\text{rms}} \frac{Z}{R} = (I_{\text{rms}})^2 Z \frac{Z}{R} = \frac{(V_{\text{rms}})^2}{Z} \frac{Z}{R}$$

P_{rms} can also be found using by using I_{\max} & V_{\max} (instead of I_{rms} & V_{rms}) and multiplying by $\frac{1}{2}$. Why? Because $I_{\text{rms}} V_{\text{rms}} = (.707 I_{\max})(.707 V_{\max}) = \frac{1}{2} I_{\max} V_{\max}$. Similarly, $(I_{\text{rms}})^2 = \frac{1}{2} (I_{\max})^2$ and $(V_{\text{rms}})^2 = \frac{1}{2} (V_{\max})^2$.

Optional: If your class studies *instantaneous power* (the rate of energy dissipation at an instant of time), use the instantaneous values of I & V : $P_{\text{instantaneous}} = I_{\text{inst}} V_{\text{inst}} (R/Z) = I_{\text{inst}}^2 Z (R/Z) = (V_{\text{inst}}^2/Z)(R/Z)$. The time-dependence of I & V is discussed in Sections 13.3-13.4.

There are many formulas, but they're just familiar dc formulas with 2 changes: replace R with Z , multiply by R/Z . Use rms-values to get P_{rms} , or use max-values and multiply by $\frac{1}{2}$. Optional: to find P_{inst} , substitute instantaneous-values.

PROBLEM 13-A

An LRC series circuit with $L = 80 \text{ mH}$, $R = 20 \Omega$, and $C = 50 \mu\text{F}$, is driven by a 60 Hz source with an average voltage of 120 V. Find the circuit's inductive reactance, capacitive reactance, impedance, maximum current, maximum voltage across each circuit element, and average power. How can you change the 's capacitance to get a "resonant circuit"?

SOLUTION 13-A

Translate words into variable-letters, choose a formula, substitute-and-solve:

$$\begin{aligned}\text{inductive reactance} &= X_L = \omega L = 2\pi f L = (2\pi)(60)(80 \times 10^{-3}) = 30.2 \Omega, \\ \text{capacitive reactance} &= 1/\omega C = 1/(2\pi f C) = 1/[(2\pi)(60)(50 \times 10^{-6})] = 53.1 \Omega, \\ \text{impedance} &= \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{20^2 + (30.2 - 53.1)^2} = 30.4 \Omega.\end{aligned}$$

From Section 13.1, $\Delta V_{S\max} = \Delta V_S \text{ rms} / .707 = (120) / .707 = 170 \text{ V}$.

$$\text{maximum current} = I_{\max} = (\Delta V_S)_{\max} / Z = 170 / 30.4 = 5.59 \text{ Coulombs/s.}$$

$$\begin{aligned}\text{maximum voltages: } \Delta V_{L\max} &= I_{\max} (X_L) = (5.59)(30.2) = 169 \text{ V}, \\ \Delta V_{R\max} &= I_{\max} (R) = (5.59)(20) = 112 \text{ V}, \\ \Delta V_{C\max} &= I_{\max} (X_C) = (5.59)(53.1) = 297 \text{ V}.\end{aligned}$$

$$\begin{aligned}P_{\text{rms}} &= I_{\text{rms}} V_{\text{rms}} (R/Z) = (.707 I_{\max})(.707 V_{\max}) (R/Z) \\ &= (.707)(5.59) (.707)(170)(20/30.4) = 313 \text{ Watts},\end{aligned}$$

$$P_{\text{rms}} = \frac{1}{2} I_{\max} V_{\max} (R/Z) = \frac{1}{2} (5.59)(170)(20/30.4) = 313 \text{ Joules/second}$$

For resonance, $\omega^2 LC = 1$, $([2\pi][60])^2 (80 \times 10^{-3})C = 1$, $C = 8.79 \times 10^{-5} \text{ F} = 879 \mu\text{F}$.

Most equations in this section are for the "cycle as a whole". If your class studies instantaneous equations (that describe what is happening at an instant of time) and the time-dependence of voltage, read optional Sections 13.3 & 13.4. {No matter what your class does, you may find it helpful to read Section 13.3, which is short, intuitive and non-mathematical.}

13.3 Time-Dependence of Voltage Maximums

Sections 12.5 and 11.10 discuss LR and RC circuits. When the switch is closed in the LR circuit below, INDUCTOR produces ΔV_L to fight the change in current. After a long time, I through ---^\wedge has reached its maximum value and ΔV_R is a maximum; $\Delta I / \Delta t = 0$ so there is no need for INDUCTOR to "fight", and $\Delta V_L = 0$. Notice the order of voltages: first the maximum ΔV_L occurs, then the maximum ΔV_R .

In the rest of Chapter 13, I'll often shorten ΔV to V , but remember that V is a potential **difference**.

When the switch first closes in the RC circuit, I and V_R are maximum. After a long time the fully charged ---^\wedge has maximum V_C , but no current flows through the ---^\wedge (or ---^\wedge) so $V_R = 0$. First V_R occurs, then V_C .

When the switch closes on the LRC circuit, maximum V_L occurs first (as INDUCTOR reacts to fight the change) but V_R and V_C are zero. Then current increases and reaches a maximum, and so does V_R . Finally the current stops because ---^\wedge is fully charged, with maximum V_C ; I is constant at zero, so V_L and V_R are zero. The order of voltage maximums is V_L , V_R and V_C : L R C.

[picture of LRC circuit will be here]

If the dc battery is replaced by an ac voltage source, current and voltages will change continuously. But the order of V-maximums is the same as in a dc circuit: first $\Delta V_{L\max}$ occurs, followed $\frac{1}{4}$ cycle later by $\Delta V_{R\max}$ -and- I_{\max} , followed $\frac{1}{4}$ cycle later by $\Delta V_{C\max}$. The relationship between these V-maximums and $\Delta V_{S\max}$ is discussed in Section 13.4.

The connection between statements (like "V_L leads I" or "I lags behind V_L") and graphs (like V_L-versus-time) can be confusing. Section 13.4 shows an easy, logical way to understand these graphs.

The order of circuit elements doesn't matter. These circuits all behave the same:
.....[there will be pictures of circuits with elements in different order: LRC, LCR, RLC, RCL, LRC, LCR, or with multiple elements of any one type, as in LRCL, LRCR, and so on].....

13.4 Phasor Diagrams, Graphs, Phase Angles, and Time-Dependent Equations

Voltage relationships can be seen easily on a *phasor diagram*. The length of the L, R and C arrows (labeled on the first diagram below) represent the magnitudes of $\Delta V_{L\max}$, $\Delta V_{R\max}$ and $\Delta V_{C\max}$, respectively. The vertical component of the L, R and C arrows (these can be called the *projections* of the arrows onto the vertical axis) show the values of V_L, V_R and V_C at a certain instant of time. The first diagram shows what is happening at the instant we define to be t + 0. Look at[picture will be here]......[this section will have more omissions because it's so "visual"]

Look at the tip of the R-arrow in the five diagrams. Do you see it make steady progress around the circle? Do you see the relationship between the height of the R-arrow's tip and height of the V_R curve? { Just as we did in Section 8.2 for *simple harmonic motion*, we can take advantage of the fact that when an object moves around a circle at constant speed, the vertical component of its position imitates a "sine wave". }

You can use this same process to understand the sine curves for V_L and V_C.

A phasor diagram is like 3 cars, spaced $\frac{1}{4}$ cycle apart, moving around circles with different radii. The V_L car peaks first, then V_R, V_C and the empty spot (with no V-arrow). This multiple-cyclic process can be described as: L R C o L R C o L R C o ...

[picture goes here]

note: If your textbook uses phasor diagrams where V is represented by the horizontal (not vertical) component of V_{max}, just substitute "horizontal" for "vertical" in my descriptions.

At any instant, current is the same in every part of a circuit. I and ΔV_R reach their maximum value at the same time; they are "in phase with each other".

The first graph below shows that[snip].....

The second graph shows that [pictures]

Study the first phasor diagram below and notice

Now look at the second phasor diagram, where

Kirchoff's law is true for "instantaneous" voltages, but not for "maximum" voltage:
 $\Delta V_{L\max} + \Delta V_{R\max} + \Delta V_{C\max} \neq \Delta V_{S\max}$.

The four main equations of Section 13.2 have the same format: $\Delta V_{\max} = I_{\max} (\)$

Don't confuse visual-mathematical symbolism with reality. In Section 8.2 the movement of a race car around a circle is used to describe *simple harmonic motion* in equations, even though the object (a block moving back and forth) is not really moving in a circle. Similarly, we can use phasor diagrams to develop equations for the time-dependence of ΔV , even though the 4 voltages don't really move in a circle like the 4 arrow-tips do. And we add V_{\max} arrows (for V_L , V_R and V_C) as vectors to get the correct $V_{S\max}$, even though voltages aren't vectors.

the Phase Angle " θ "

If we define $t + 0$ when V_L is maximum (as in the earlier phasor diagrams) and $\theta + 0$ as the location of V_R at this time, then θ gives the angular position of V_S at this $t + 0$ instant, and θ is a *phase angle*. θ and θ are defined the same as in Section 8.2 !

In the first diagram below, drawn at $t + 0$ when V_R is maximum, $V_{L\max}$ is larger than $V_{C\max}$ so the V_S arrow is ahead of the V_R arrow, and θ is + .

In the second diagram, $V_{C\max}$ is larger than $V_{L\max}$; V_S is behind V_R and θ is - .

ΔV_L fights and delays the buildup of current. It is the deciding factor if $\Delta V_{L\max}$ is larger than $\Delta V_{C\max}$, as in the first diagram; this causes the maximum of I-and- V_R to occur after the maximum of V_S .

The effect of ΔV_C is opposite that of ΔV_L . In the second diagram ΔV_C is the most important factor, so its "anti-delay" makes I_{\max} (and $\Delta V_{R\max}$) occur before $\Delta V_{S\max}$. Because of the way θ is defined, instead of saying " $V_{R\max}$ is ahead of $V_{S\max}$ " we can state the same fact as " $V_{S\max}$ is behind $V_{R\max}$ ", which means that θ is - .

[diagrams will be here]

As described earlier, the V_{\max} -triangle and XRZ-triangle have the same shape and same θ , so we could draw the analogous XRZ (instead of V_{\max}) triangle and use this same "ahead or behind" logic to reach the following useful conclusions.

When X_L is larger than X_C , the circuit's reactance is "inductive" and θ is + .

When X_C is larger than X_L , the circuit's reactance is "capacitive" and θ is - .

When X_L equals X_C , the circuit is "resonant" with no reactance, and θ is zero.

" $\theta = \tan^{-1} [(X_L - X_C) / R]$ " gives the correct θ , including the correct \pm sign.

Time-Dependent Equations

To understand the equations below, think about this step-by-step derivation:

Each $V_{\text{instantaneous}}$ is the vertical component of the V_{\max} phasor arrow,
so $V_{\text{instantaneous}} = V_{\max} \sin[\text{angular } \theta\text{-position of } V_{\max} \text{ phasor arrow}]$.

(θ -position of arrow) = $\omega t + \theta_i$, where θ_i is the position when $t + 0$.

When $t + 0$, the V_L -arrow is at $+\frac{1}{2} \pi$, V_R -arrow is at 0 , V_C -arrow is at $-\frac{1}{2} \pi$,
 V_S -arrow is at $+\theta$, and I (which is in-phase with the V_R -arrow) is at 0 .

$$\begin{aligned}
 \Delta V_L &= \Delta V_{L\max} \sin(\omega t + \frac{1}{2}\pi) = +\Delta V_{L\max} \cos(\omega t) \\
 \Delta V_R &= \Delta V_{R\max} \sin(\omega t) \\
 \Delta V_C &= \Delta V_{C\max} \sin(\omega t - \frac{1}{2}\pi) = -\Delta V_{C\max} \cos(\omega t) \\
 \Delta V_S &= \Delta V_{S\max} \sin(\omega t + \phi) \\
 I &= I_{\max} \sin(\omega t)
 \end{aligned}$$

These equations can be "linked" with all equations from Section 13.2 that contain $\Delta V_{L\max}$, $\Delta V_{R\max}$, $\Delta V_{C\max}$, $\Delta V_{S\max}$ or I_{\max} . Also, $\omega = 2\pi f$.

If your textbook uses horizontal (not vertical) components of the V-arrows, or if it defines $t+0$ at a different time (for example, when V_S is a maximum), its equations will differ from the equations above. But the basic principles are identical, and when used correctly either set of equations will give correct answers.

13.90 Memory-Improving Flash Cards

- 13.1 In a dc circuit, electrons ____.
In an ac circuit, electrons ____.
- 13.1 The shape of a V(or I)-versus-t graph is ____.
- 13.1 $V_{rms} = \text{____}$, so $V_{\max} = \text{____}$. $I_{rms} = \text{____}$.
 $.707 V_{\max}$, $V_{rms}/.707$, $.707 I_{\max}$
- 13.2 The rest of Chapter 13 describes the ____.
- 13.2 Maximum values of V_L , V_R & V_C occur at ____.
At every instant, current is ____.
- 13.2 V_{\max} equations for L, R, C & S have form ____,
where [] is ___, which all have ____.
____ and ____ both contribute to ___,
which indicates ____.
- 13.2 An inductor has large ΔV_L when it ___,
and impedes most when ___, so ___.
A capacitor has near-max ΔV_C when it ___,
and impedes most when ___, so ___.
At ___ frequency, ___ is most important. (2)
- 13.2 If ac circuit is missing LRC elements, ____.
- 13.2 Max ___ occurs at min ___, which is called ____.
This occurs when ____.
___ is larger than ___. To convert, ___ or ___.
- always move in the same direction
alternate directions (oscillate back & forth)
sine wave (is assumed for all of Chapter 13)
behavior of a series LRC circuit
different times
equal in every part of a series circuit
 $\Delta V_{\max} = I_{\max} []$
 X_L , R, X_C or Z ; same units (ohms, Ω)
reactance-X's, resistance-R, impedance-Z
how much a circuit impedes ac current flow
fights against current-changes
large L and high f, $X_L = \omega L$
is close to holding its full charge
small C and low f, $X_C = 1/\omega C$
high, L ; low, C
substitute $L = 0$, $R = 0$, $C = \infty$
 I_{\max} , Z , resonance
 $X_L = X_C$, $\omega^2 LC = 1$, $\omega = \sqrt{1/LC}$
 ω , f, $\omega = 2\pi f$, $\omega / 2\pi = f$

13.2 In LRC, ___ dissipates energy, ___ energy.

13.2 To get P-formulas, use __, then __
___, which is the ___.

To get $P_{\text{root-mean-square}}$, substitute ___ or ___.
Optional: To get $P_{\text{instantaneous}}$, substitute ___.

~^~  & INDUCTOR, store & release

$P = IV = I^2 R = V^2/R$, replace R by Z
multiply by R/Z, power factor

rms-values, max-values and multiply by $\frac{1}{2}$
instantaneous-values

13.3 V_{\max} order: in LR __, in RC __, in LRC __.
Starting with __, there is ___ between ___.
Circuit behavior doesn't depend on the ___.

is L R, is R C, is L R C
 V_L , $\frac{1}{4}$ cycle ($\frac{1}{4} T$, 90° , $\pi/2$ rads), V_{\max} 's
order of circuit elements

13.4 A phasor diagram is analogous to ___.
If V_S is also drawn, there are ___ that are ___.

13.4 At any instant ___ is same thru circuit, ___ aren't.
___ are always in phase. V-cycle is ___.

13.4 V_{\max} is ___, $V_{\text{instantaneous}}$ is ___.

phasor & graph: same ___ for ___ & ___.

13.4 To interpret graph correctly, ask ___ not ___.

13.4 ___ = ___ for ___ but not for ___.

13.4 right triangle: legs are ___, hypotenuse is ___,
or legs are ___, hypotenuse is ___.
These triangles (___) are ___ so they have ___.

13.4 I_{\max} always occurs after ___ and before ___.

If ___ (so ___), $V_{S\max}$ occurs ___ I_{\max} , ϕ is ___.
{ repeat for 3 possibilities }

3 race cars ($\frac{1}{4}$ cycle apart, different radii)
4 "cars", located at the tip of each arrow
current (I), potential differences (ΔV 's)
 I and V_R , L R C o L R C o L R C o ...
arrow's length, arrow's vertical component
(or horizontal component if your class...)
height, arrow-tip, V-on-graph

which peak occurs first? who wins race?

$V_L + V_R + V_C = V_S$, inst-V, max-V

($V_{L\max} - V_{C\max}$) and $V_{R\max}$, $V_{S\max}$
($X_L - X_C$) and R , Z
 V_{\max} & XRZ , similar, same ϕ

$V_{L\max}$, $V_{C\max}$

$X_L > X_C$, $V_{L\max} > V_{C\max}$, before, +
 $X_C > X_L$, $V_{C\max} > V_{L\max}$, after, -
 $X_L = X_C$, $V_{L\max} = V_{C\max}$, at same t as, 0

Eventually, Chapter 13 will be "finished" in a camera-ready format.